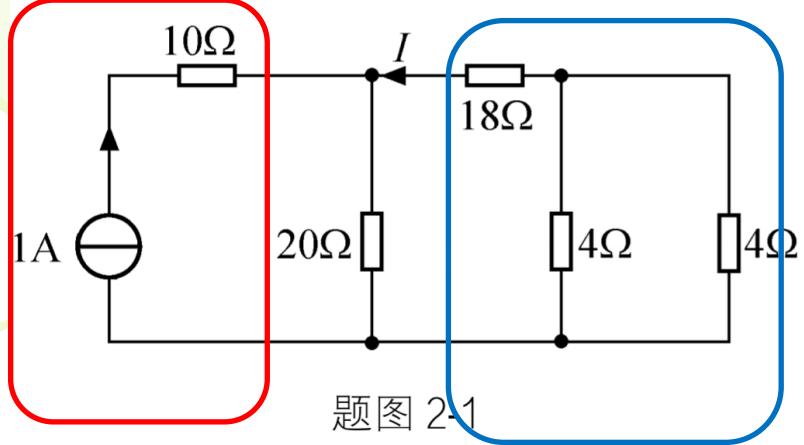



2-1 求题图 2-1 所示电路的电流  $i$ 。



解：先进行等效变换：

红色部分： 电流源和电阻串联等效为1A电流源



蓝色部分： 电阻 $4//4+18=20\Omega$

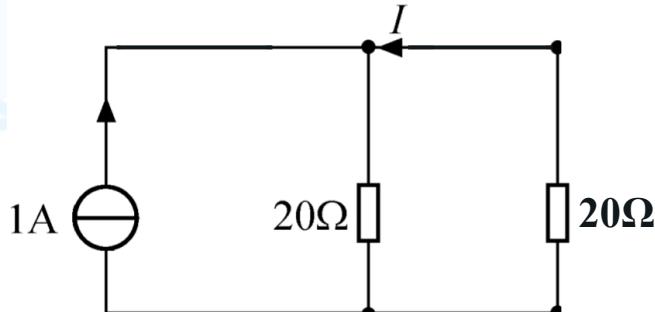



题图 2-1

$$I = -1 \times \frac{20}{20+20} = -0.5A$$

## 2-3求等效电阻R<sub>ab</sub>

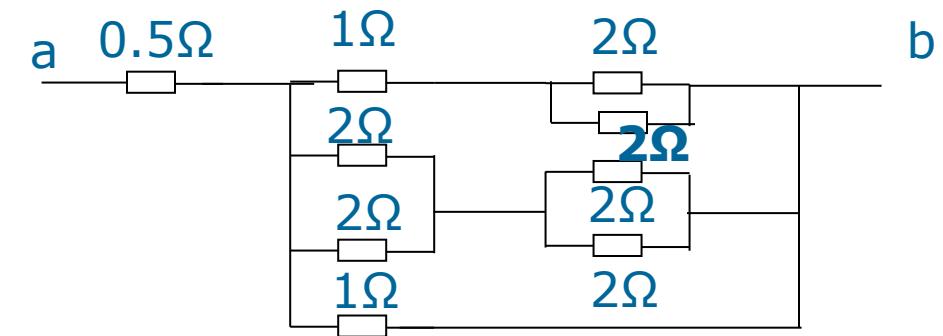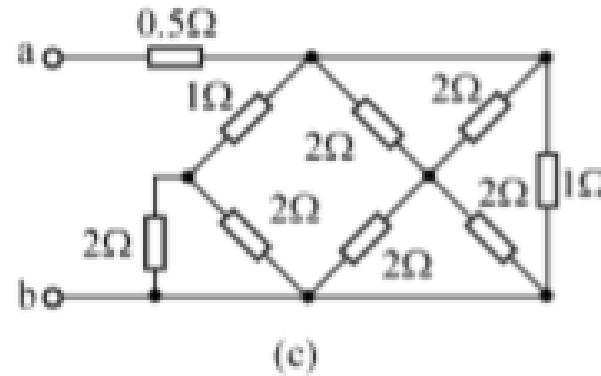

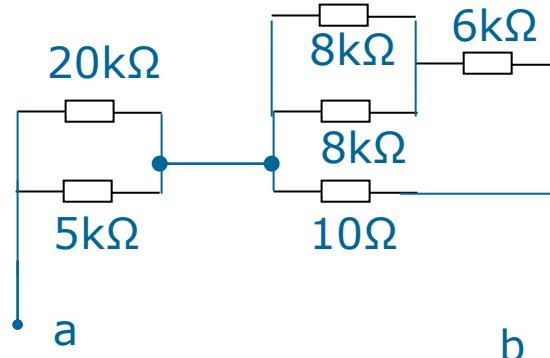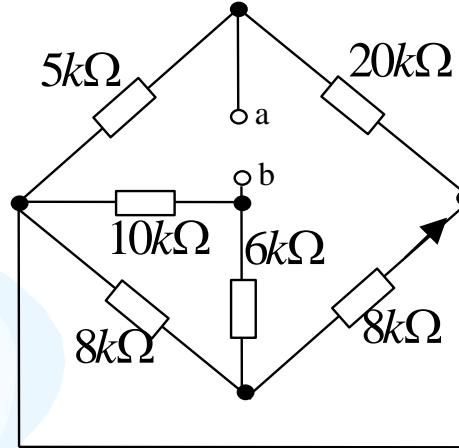
(c)  $R_{ab} = 0.5 + 1 // (1 + 2 // 2) // (2 // 2 + 2 // 2) = 1\Omega$



解d

**(d)**由图可得:  $R_{ab} = 5 // 20 + 10 // [8 // 8 + 6] = 9k\Omega$

2-5 C

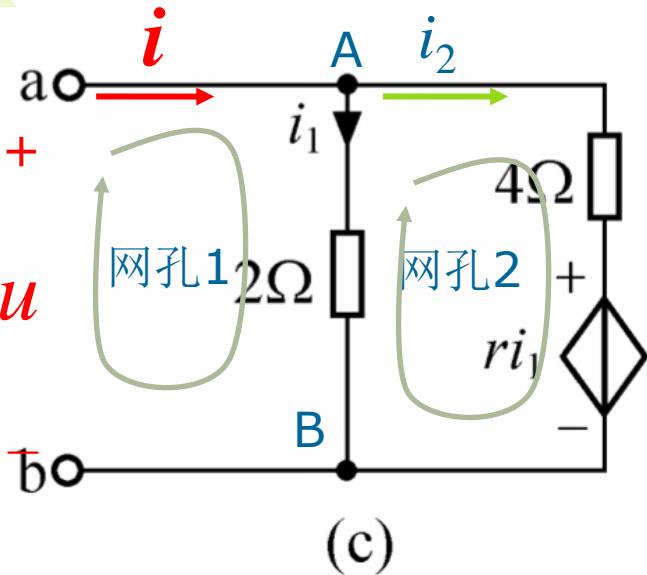

仅含受控源和电阻的电路最终等效成一个电阻。设端口上的电压为  $u$ , 电流为  $i$ , 方向如图所示, 取关联参考。

对网孔1 (广义回路) 列KVL方程:  $u = 2i_1$

网孔2列KVL方程:  $-2i_1 + 4i_2 + ri_1 = 0$

对节点A列些KCL方程:  $i_1 + i_2 - i = 0$


得

$$R_{ab} = \frac{u}{i} = \frac{8}{6-r}$$

**2-7** 电路如题图2-10所示, (1)若 $U_2=10V$ , 求电流 $I_1$ 和电源电压 $U_s$ ; (2)若 $U_s=10V$ , 求电压 $U_2$ 。

解: (1)  $I_2 = \frac{U_2}{20} = 0.5A$

$$U_3 = I_2(10 + 20) = 15V$$

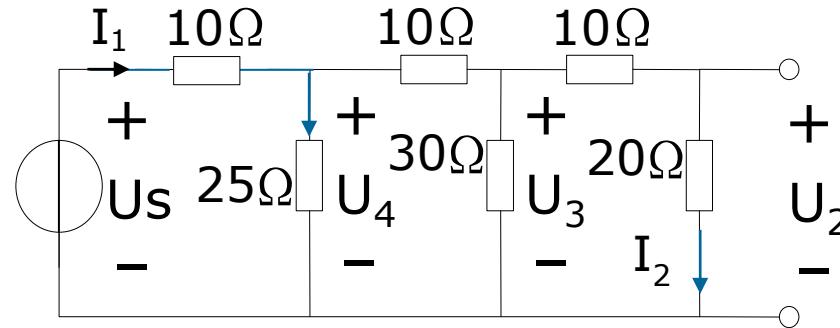

$$U_4 = \left( \frac{U_3}{30} + I_2 \right) \times 10 + U_3 = 25V \quad \therefore I_1 = \frac{U_4}{25} + \frac{U_3}{30} + I_2 = 2A$$





$$U_s = I_1 \times 10 + U_4 = 45V$$


(2)  $I_1 = \frac{U_s}{10 + 25 // [10 + 30 // (10 + 20)]} = \frac{10}{22.5} A$

$$\therefore I_2 = \frac{10}{22.5} \times \frac{25}{25 + [10 + 30 // (10 + 20)]} \times \frac{25}{30 + 10 + 20} = \frac{10}{22.5} \times \frac{1}{2} \times \frac{1}{2} = \frac{1}{9} A$$


$$U_2 = I_2 \times 20 = \frac{20}{9} V$$

## 2-8 化简电路

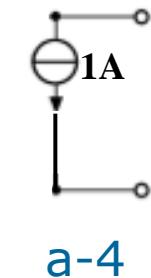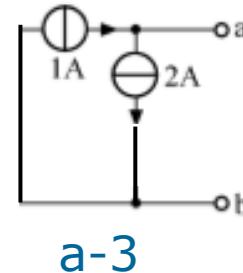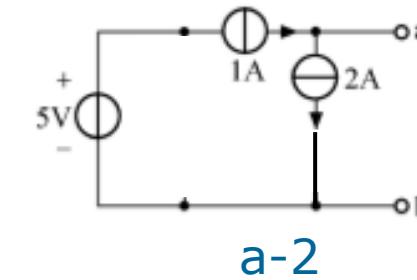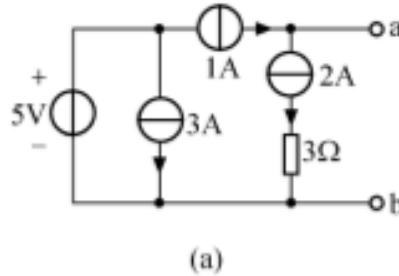


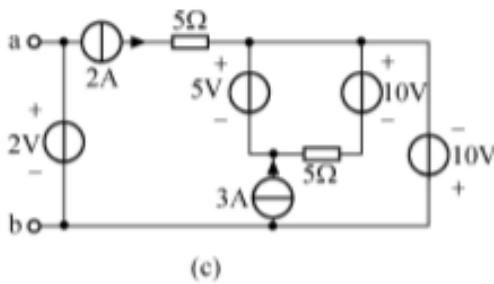


(c)

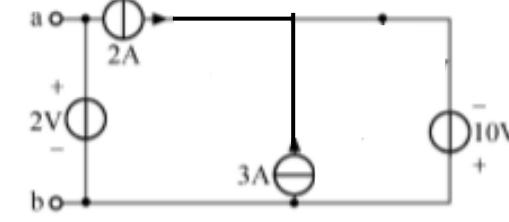


c-2

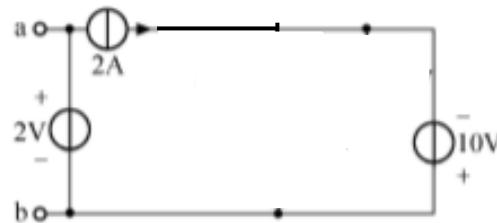

c-3

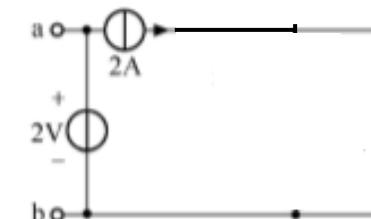


c-4

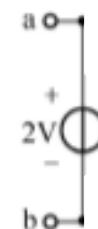


c-5


## 2-9C 化简电路为戴维南等效电路

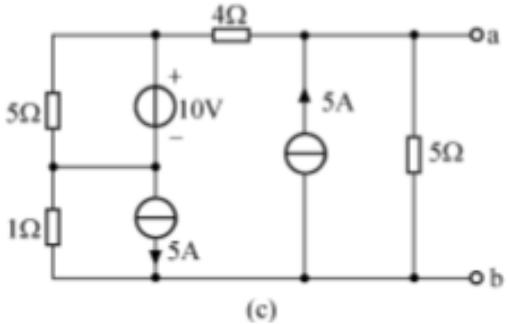


(c)

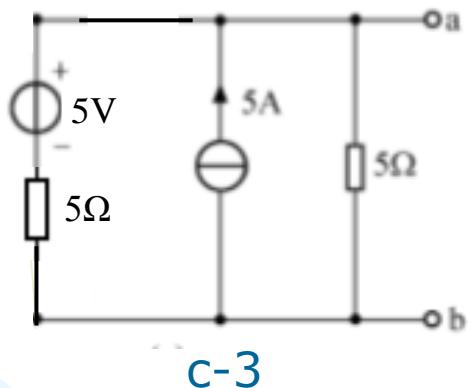


c-3

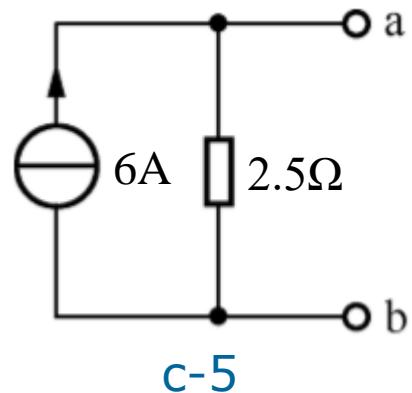


c-5

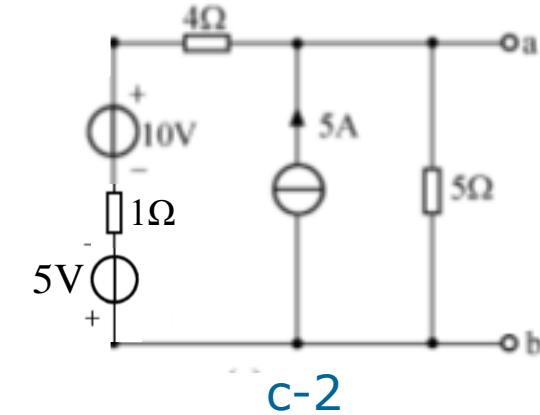

c-2

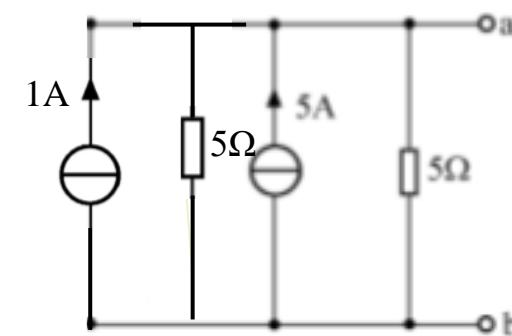


c-4

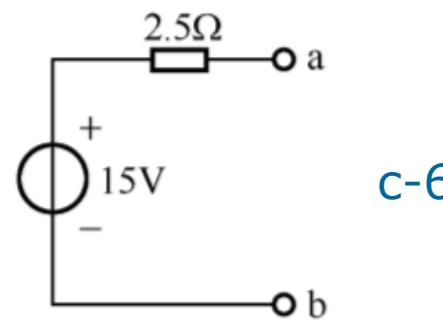


c-6

2-10 (b)

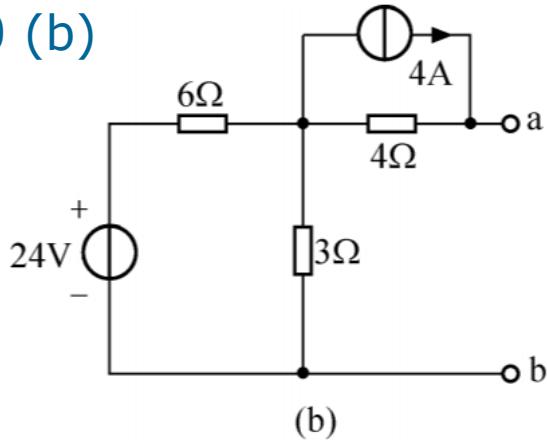


(b)

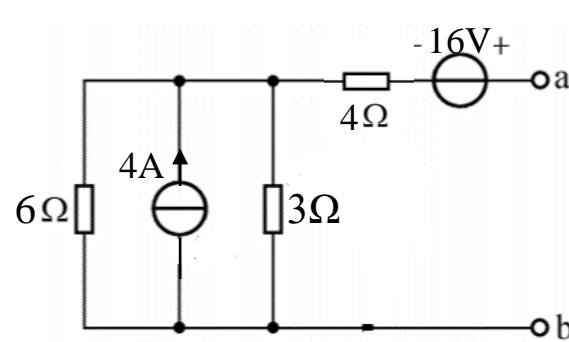


$$3//6=2\Omega$$


b-1

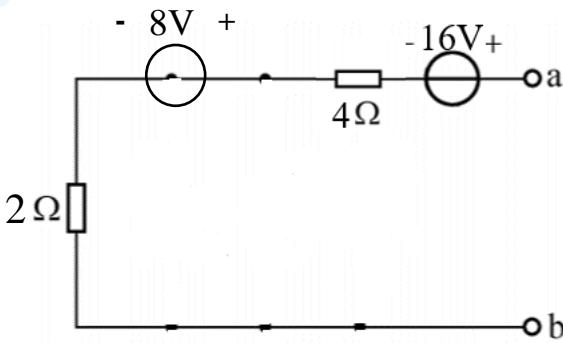

b-2




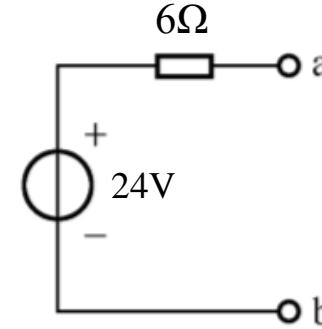


b-3

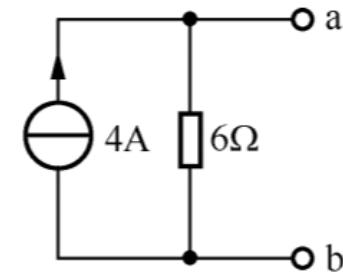


b-4

## 2-15 (a) 化简电路为戴维南等效电路

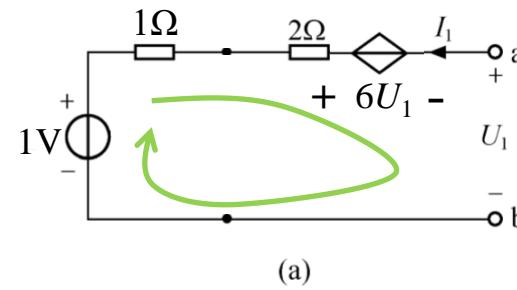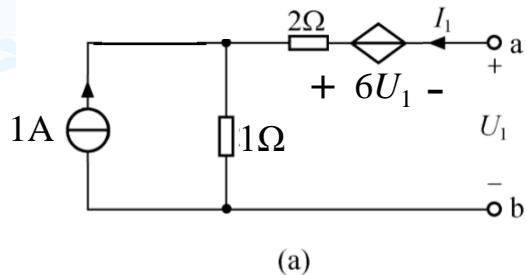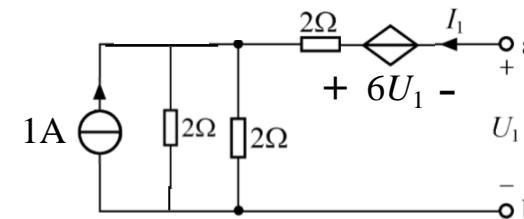
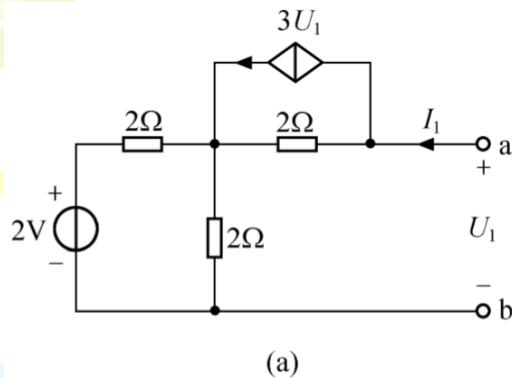


$$U_1 - 1 - 3I_1 + 6U_1 = 0$$

$$U_1 = \frac{1}{7} + \frac{3}{7} I_1$$

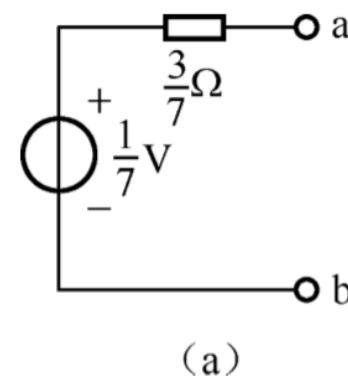

2-15(b)

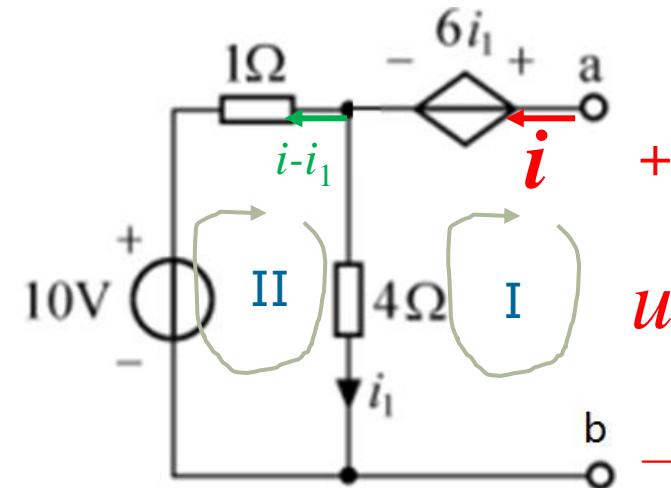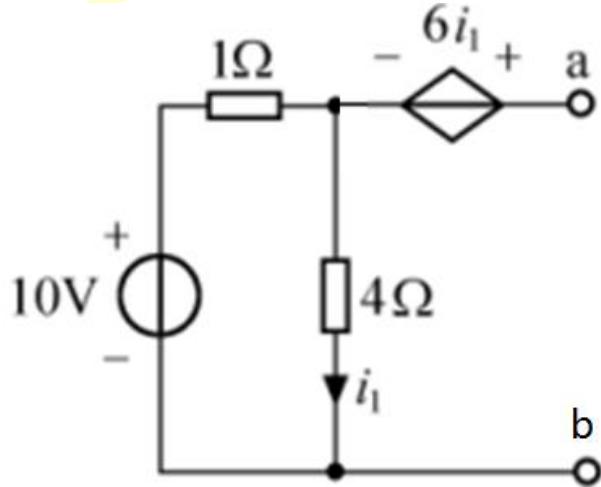


设端口上的电压电流如果所示参考方向


$$\text{I网孔: } u - 4i_1 - 6i_1 = 0$$

$$\text{II网孔: } 4i_1 - 10 - (i - i_1) = 0$$

$$\text{消去} i_1: u = 2i + 20$$

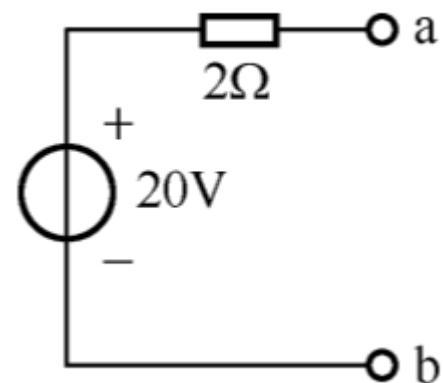


戴维南电路

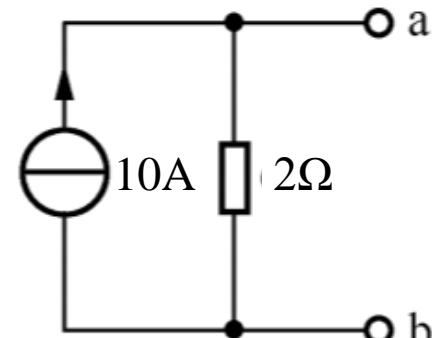


诺顿电路

2-16b 化为诺顿等效电路

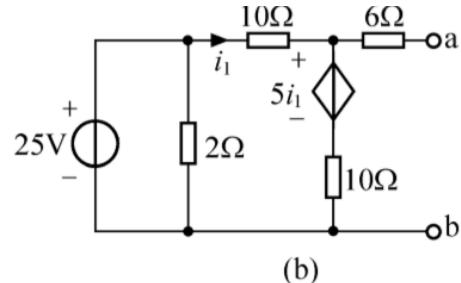

电路等效为

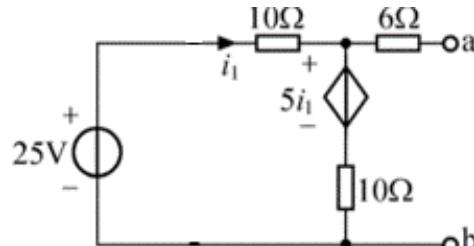




解法1 加压求流法

$$-25 + 10i_1 + 5i_1 + 10i_2 = 0$$


$$u - 10i_2 - 5i_1 - 6i = 0$$

$$i_2 - i_1 - i = 0$$


$$u = 10i + 15$$

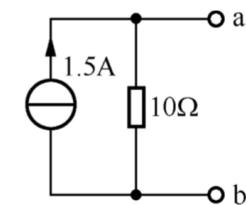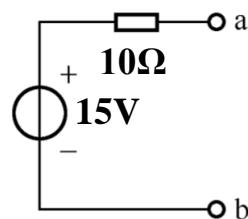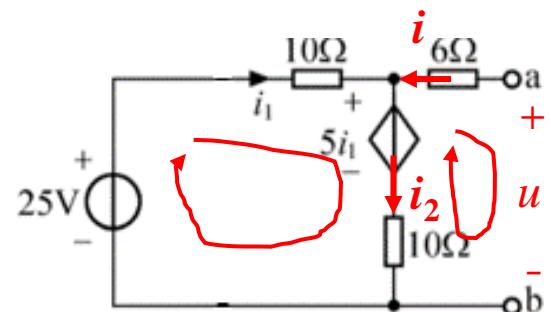


2-16b 化为诺顿等效电路

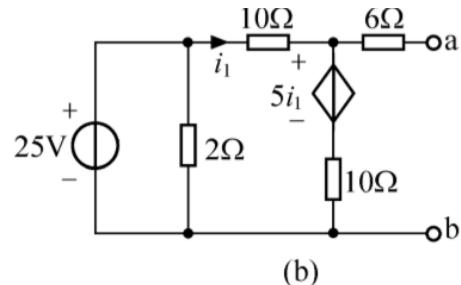


1.求 $i_{sc}$

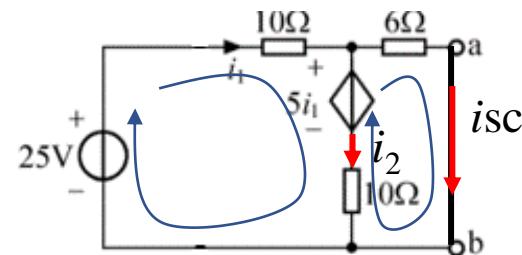

2求等效电阻 $R_0$ , 加压求流法

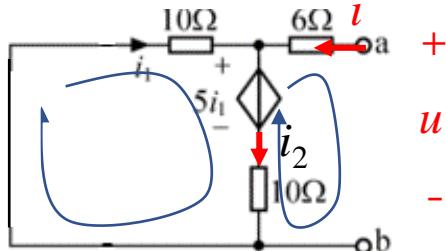

电路等效为

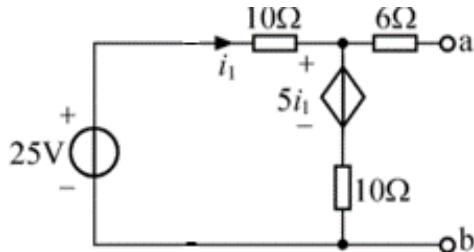

解法2：第四章诺顿定理：  
对两网孔列些KVL方程

$$-25 + 10i_1 + 5i_1 + 10i_2 = 0$$

$$6i_{sc} - 10i_2 - 5i_1 = 0$$

对节点列些KCL

$$-i_1 + i_2 + i_{sc} = 0$$

得  $i_{sc} = 1.5A$

设端口电流为 $i$ , 电压为 $u$

对两回路列些KVL, 对节点列些KCL

$$\text{得 } R_0 = 10\Omega$$

$$10i_1 + 5i_1 + 10i_2 = 0$$

$$-6i + u - 10i_2 - 5i_1 = 0$$

$$-i - i_1 + i_2 = 0$$

