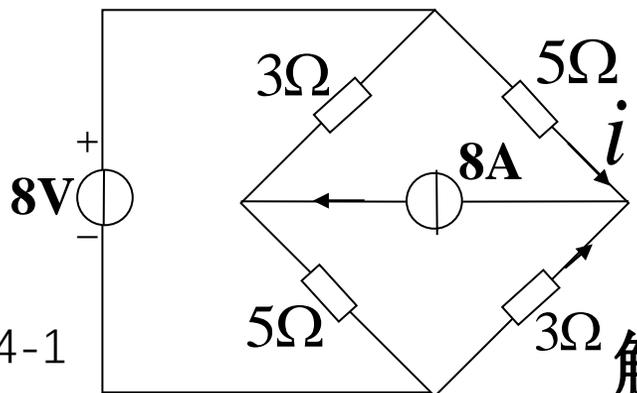



4-1. 电路如题图4-1所示，试用叠加定理求电流*i*。



题图4-1(a)

题图4-1

解：利用叠加定理：

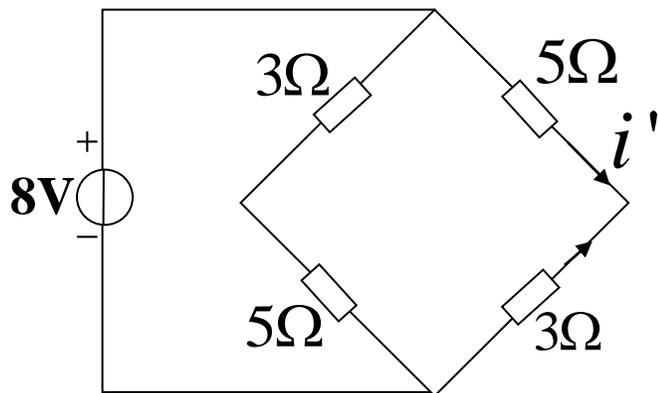

题图4-1(b)

(1) 当电压源单独作用时，


$$i' = \frac{8}{3+5} = 1A$$

(2) 当电流源单独作用时，

$$i'' = \frac{3}{3+5} \times 8 = 3A$$


(3) 总电流为：

$$i = i' + i'' = 4A$$

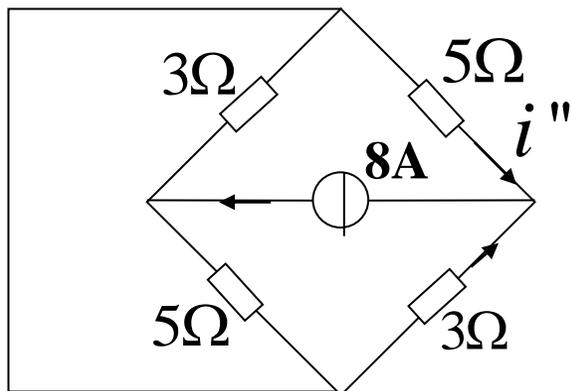

4-5 (1) 题图 4-5 所示的线性网络 N 只含电阻。若 $i_{S1} = 8A$, $i_{S2} = 12A$ 时, $u_x = 80V$; 若 $i_{S1} = -8A$, $i_{S2} = 4A$ 时, $u_x = 0V$ 。当 $i_{S1} = i_{S2} = 20A$ 时, u_x 为多少? (2) 若所示网络 N 含有独立源, 当 $i_{S1} = i_{S2} = 0$ 时, $u_x = -40V$; 所有 (1) 中的数据仍有效。当 $i_{S1} = i_{S2} = 20A$ 时, 电压 u_x 为多少?

解: (1) 由线性网络的齐次性和叠加性, 可设:

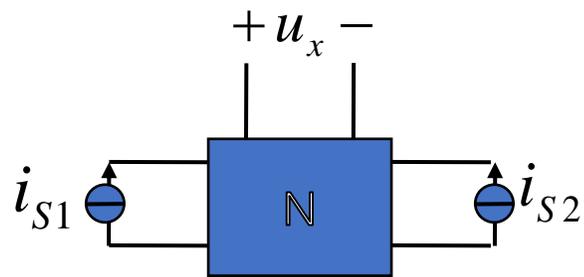

$$u_x = k_1 i_{S1} + k_2 i_{S2}$$

代入已知条件, 有:

$$\begin{cases} 8k_1 + 12k_2 = 80 \\ -8k_1 + 4k_2 = 0 \end{cases} \therefore k_1 = 2.5, k_2 = 5$$


当 $i_{S1} = i_{S2} = 20A$ 时, $u_x = 2.5 \times 20 + 5 \times 20 = 150V$

(2) 当网络N含有独立电源时，设其所有独立电源的作用为 $\sum p_n e_n$ ，则：

$$u_x = p_1 i_{S1} + p_2 i_{S2} + \sum p_n e_n$$

将 $i_{S1} = i_{S2} = 0A$ 时， $u_x = -40V$ 代入：

$$\sum p_n e_n = -40$$

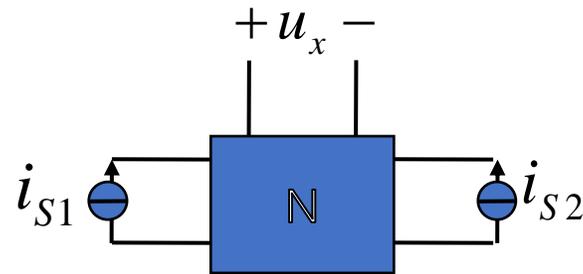


再将 (1) 中的条件代入，有：

$$\begin{cases} 8p_1 + 12p_2 - 40 = 80 \\ -8p_1 + 4p_2 - 40 = 0 \end{cases} \quad \therefore p_1 = 0, p_2 = 10$$


故，当 $i_{S1} = i_{S2} = 20A$

$$u_x = 0 \times 20 + 10 \times 20 - 40 = 160V$$


4-9(a). 试求题图4-9所示二端网络的戴维南等效电路。

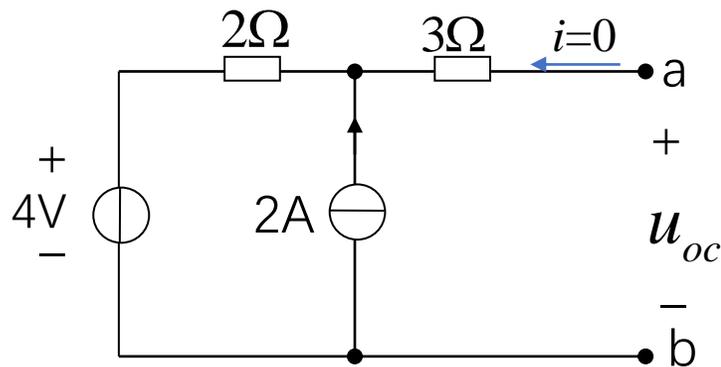

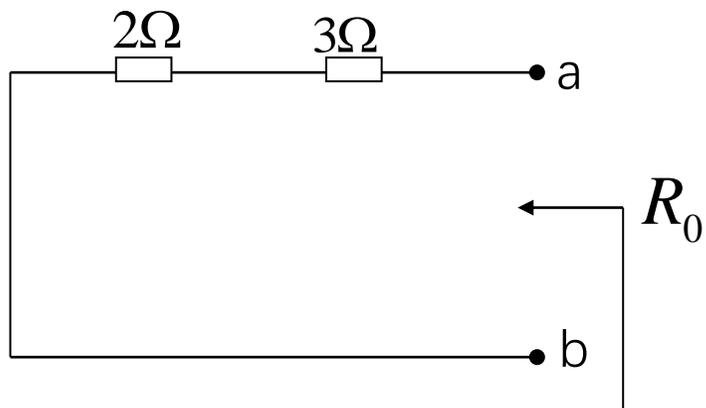
解：根据戴维南定理： $u_{oc} = 2 \times 2 + 4 = 8V$



$$R_0 = 5\Omega$$

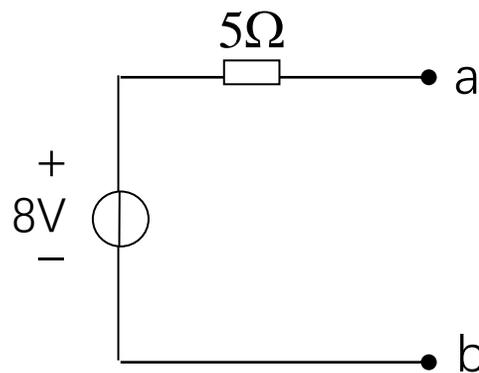

4-10(b) 试求题图4-10所示二端网络诺顿等效电路。

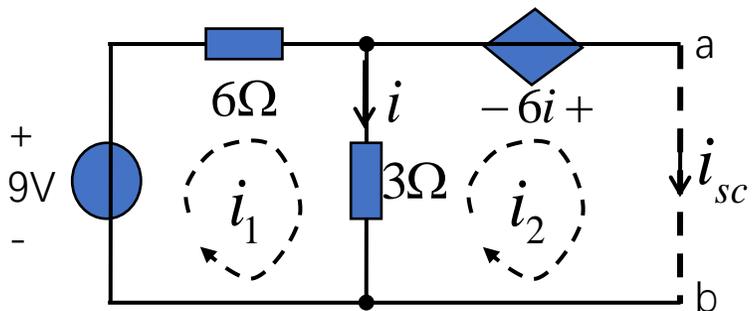



解： (1) 先求短路电流 i_{sc} ：令端口ab短路，网孔法有：

$$\begin{cases} 9i_1 - 3i_2 = 9 \\ -3i_1 + 3i_2 = 6i \end{cases} \quad \therefore i_{sc} = i_2 = 1.5A$$

$$i = i_1 - i_2$$

另解：短路电流 i_{sc} ：

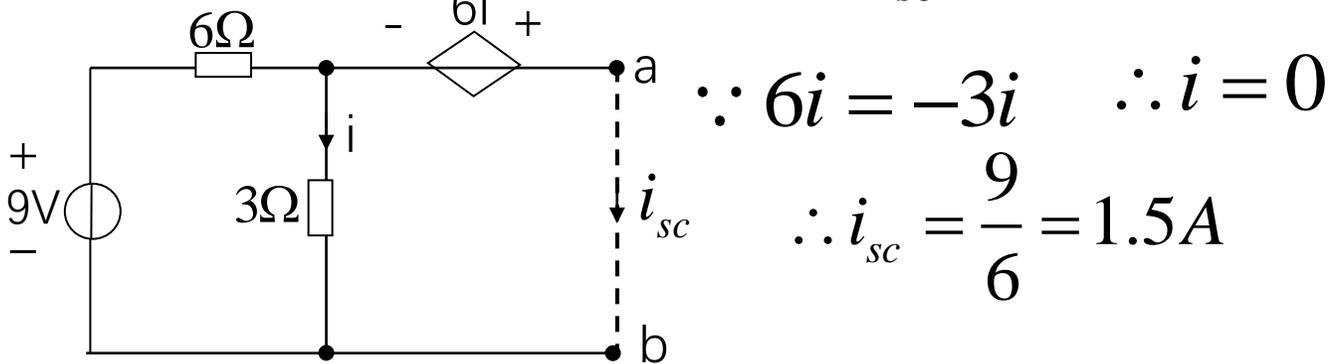

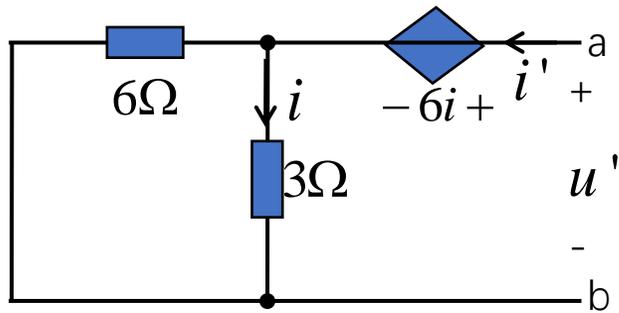


(2) 求输出电阻 R_0 : 令独立电压源短路:

加压求流法, 设端口电压为 u' , 电流为 i'


(注: 设的端口电流与受控源控制量 i 不能相同)

$$\begin{cases} u' = 6i + 3i = 9i & \therefore u' = 9 \times \frac{6}{6+3} i' = 6i' \\ i = \frac{6}{6+3} i' & R_0 = 6\Omega \end{cases}$$


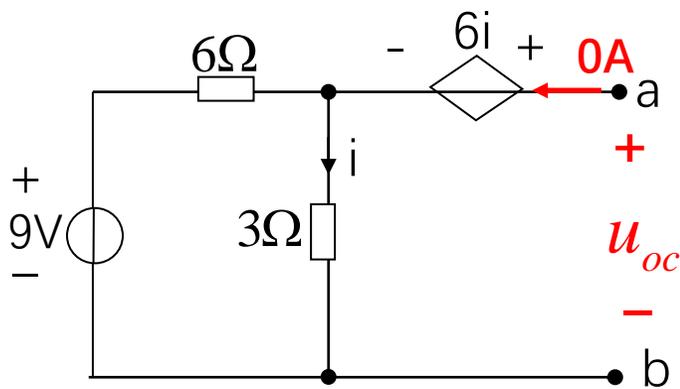
另解 开短路法, 求开路电压 U_{oc} , 方向为 $a \rightarrow b$:


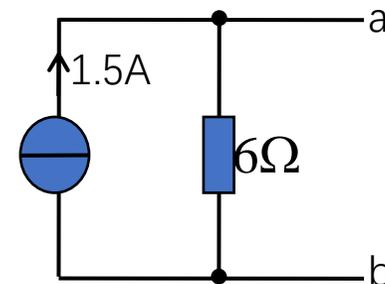
$$\begin{aligned} u_{oc} &= 6i + 3i = 9i \\ i &= \frac{9}{6+3} = 1A & \therefore u_{oc} &= 9V \\ \therefore R_0 &= \frac{u_{oc}}{i_{sc}} = 6\Omega \end{aligned}$$



4-11 用戴维南定理求题图4-11电路的电压 u

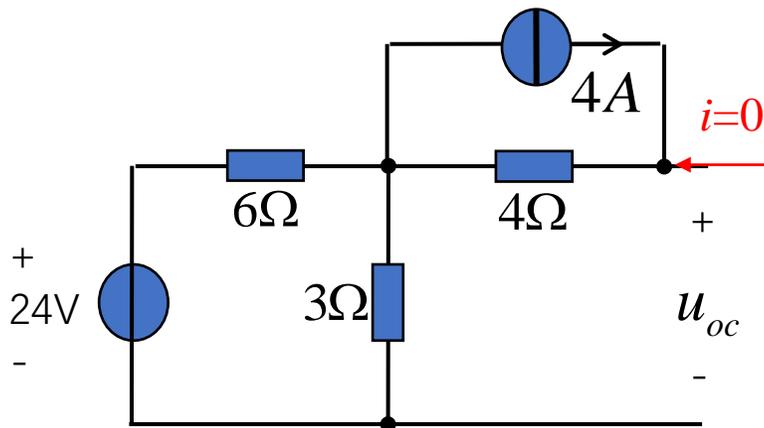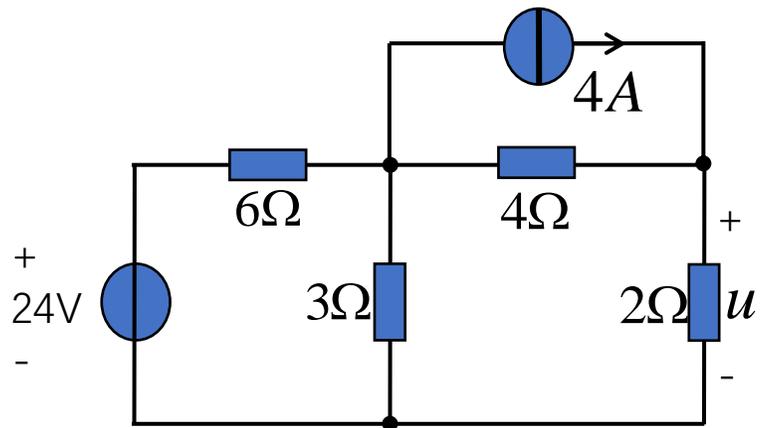



解 (1) 求开路电压 u_{oc}

$$u_{oc} = 4 \times 4 + 24 \times \frac{3}{6+3} = 24V$$

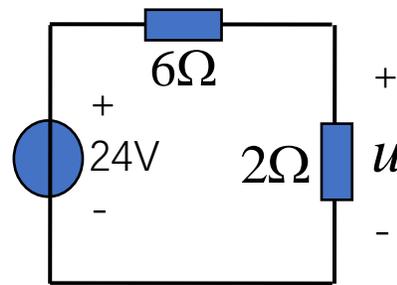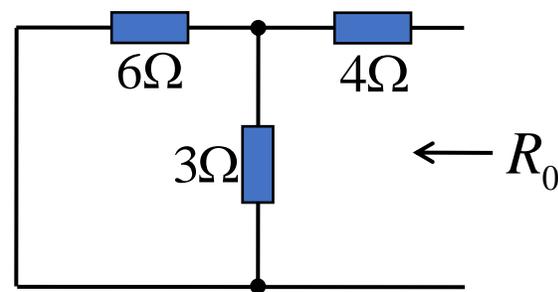
(2) 求输出电阻 R_0

$$R_0 = 6 // 3 + 4 = 6\Omega$$

$$\therefore u = 24 \times \frac{2}{6+2} = 6V$$



4-14 电路如题图 4-14 所示, 其中电阻 R_L 可调, 试问 R_L 为何值时能获得最大功率? 最大功率为多少?

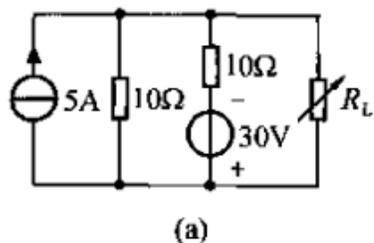

题图 4-14

(a) 解: 先求 R_L 以左部分电路的戴维南等效电路。首先求开路电压 u_{oc} , 如解图 4-14 (a) - (1) 所示, 有


$$u_{oc} = 5 \times (10 // 10) - 30 \times \frac{10}{10 + 10} = 10V$$

再求等效电阻 R_o , 如解图 4-14 (a) - (2) 所示, 有


$$R_o = 10 // 10 = 5\Omega$$

题图 4-14 (a) 负载 R_L 以左部分电路可用其对应的戴维南等效电路替代, 如解图 4-14 (a) - (3) 所示。因此, 当 $R_L = R_o = 5\Omega$ 时可获得最大功率, 此最大功率为


$$P_{max} = \frac{u_{oc}^2}{4R_o} = \frac{10^2}{4 \times 5} = 5W$$

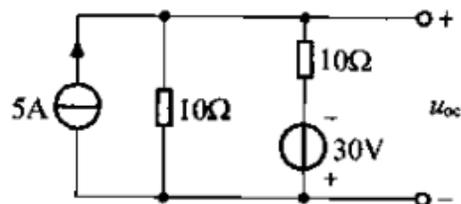

解图 4-14 (a) - (1)

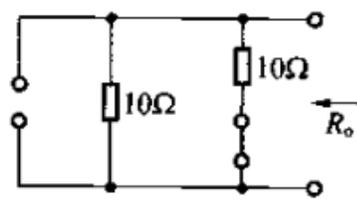


解图 4-14 (a) - (2)

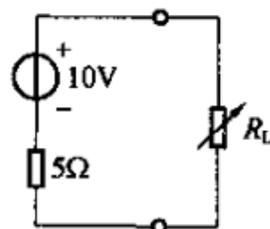

解图 4-14 (a) - (3)

4-14(b) 电路如题图4-14所示，其中电阻 R_L 可调，试问 R_L 为何值时能获得最大功率？最大功率为多少？

解：将 R_L 左端电路化为戴维南等效电路：

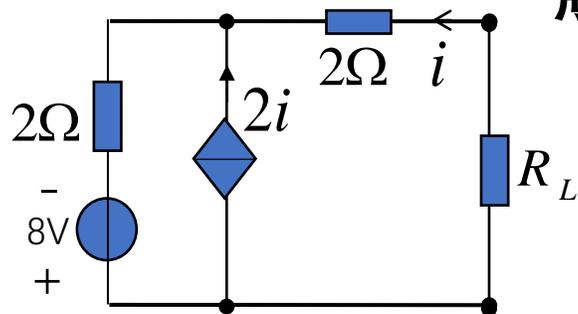


(1) 先求开路电压 u_{oc}


$$\because i = 0$$

$2i$ 的受控电流源为 0 相当于开路

$$u_{oc} = -8V$$

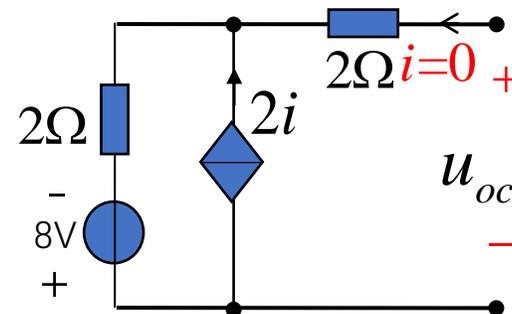

(2) 求输出电阻 R_0 令电压源短路，则：

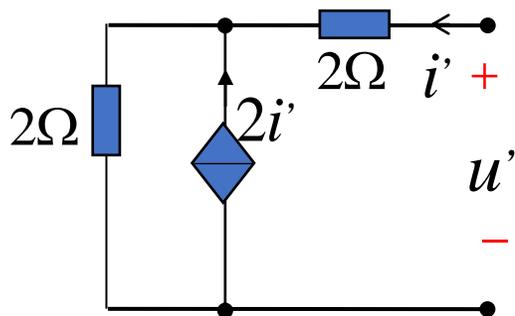

$$u' = 2i' + (2i' + i') \times 2 = 8i'$$


$$\therefore R_0 = 8\Omega$$

(3) 求最大功率：当 $R_L = R_0$ 时有最大功率，为：

$$p_{\max} = \frac{u_{oc}^2}{4R_0} = \frac{(-8)^2}{4 \times 8} = 2W$$

没布置，可以看一下。

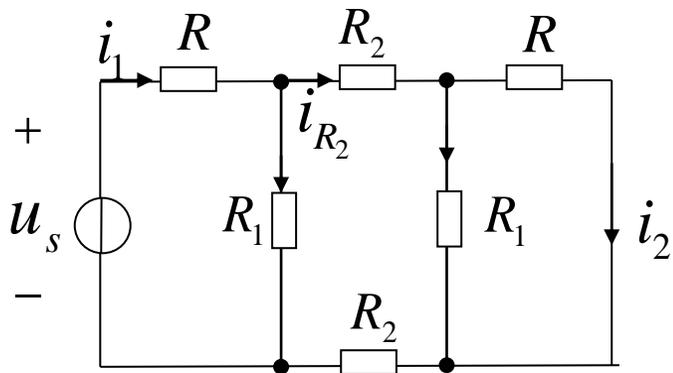
4-19 在题图4-19电路中，已知 $i_1 = 2A, i_2 = 1A$ ，
若把电路中间的 R_2 支路断开，试问此时电流 i_1 为多少？



解一：(1) 断开前：

$$i_1 - \frac{u_s - i_1 R}{R_1} = i_{R_2} = i_2 + \frac{i_2 R}{R_1}$$

$$\therefore u_s = R_1 + R$$

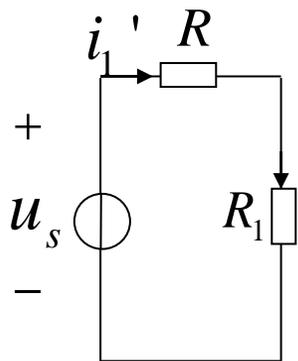


(2) 断开后：


$$u_s = i_1' (R_1 + R)$$

$$\therefore i_1' = 1A$$

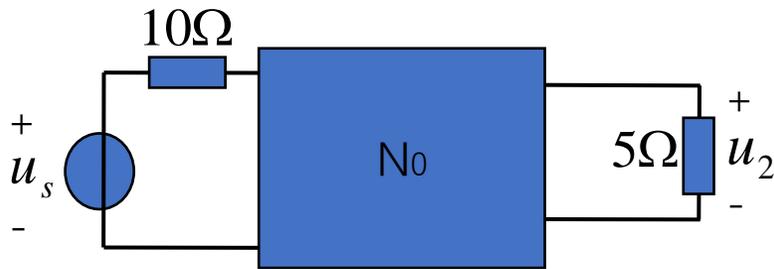4-20 线性无源二端网络 N_0 仅由电阻组成，如4-20(a)所示。当 $u_s = 100$ 时， $u_2 = 20V$ ， 求当电路改为图(b)时的电流 i 。





(a)

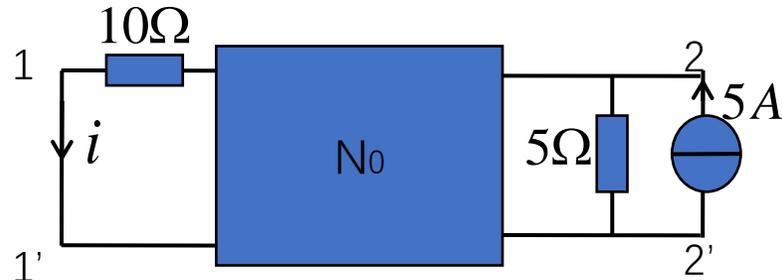


(b)

解：应用互易定理形式三+线性网络的齐次性，有：

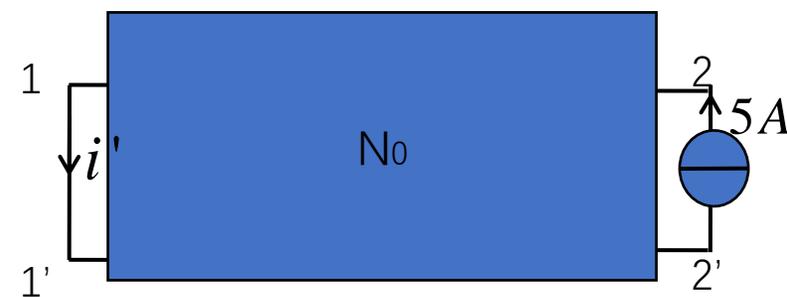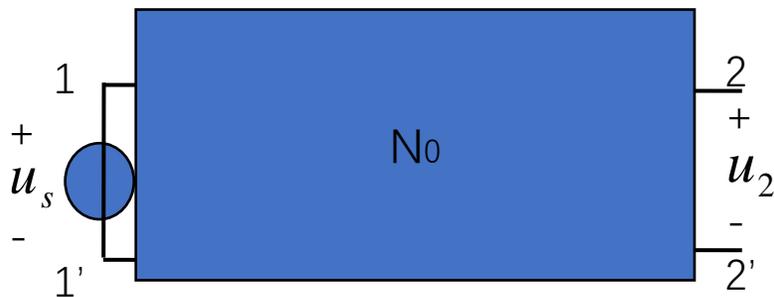

$$\frac{u_2}{u_s} = \frac{i'}{i_s'} \quad \therefore i = i' = i_s' \cdot \frac{u_2}{u_s} = 1A$$

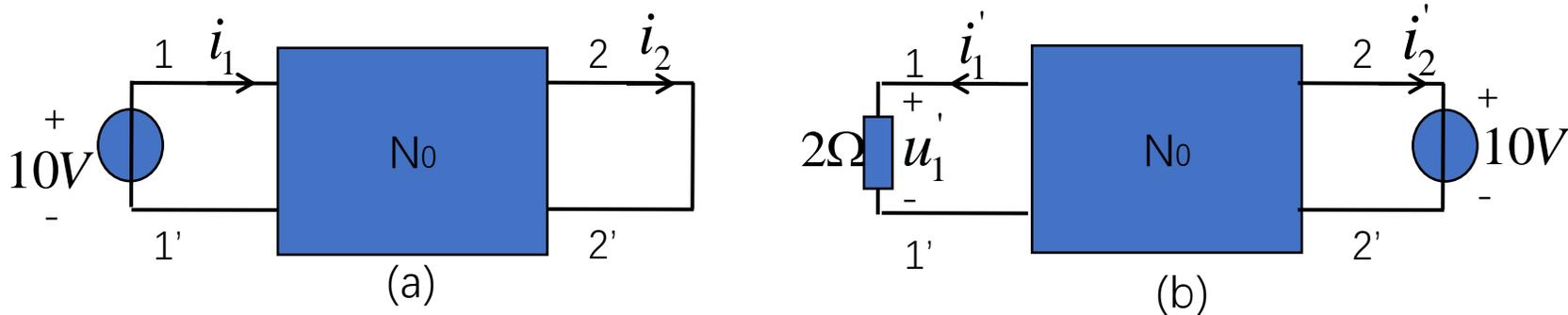4-21 题图4-21(a)中 N_0 为仅由电阻组成的无源线性网络，当10V电压源与1、1'端相接，测得输入电流 $i_1 = 5A$ ，输出电流 $i_2 = 1A$ ；若把电压源移至2、2'端，且在1、1'跨接 2Ω 电阻如图(b)所示，试求 2Ω 电阻上的电压 u_1



解： 根据特勒根第二定理，有：

$$u_s i_1' + u_2 i_2' = u_1' (-i_1) + u_s' i_2$$

$$\because u_2 = 0, u_1' = 2i_1', u_s = u_s' = 10, i_1 = 5A, i_2 = 1A$$

$$\therefore 10i_1' = 2i_1'(-5) + 10 \times 1$$

$$\therefore i_1' = 0.5A \quad \text{则：} \quad u_1' = 1V$$