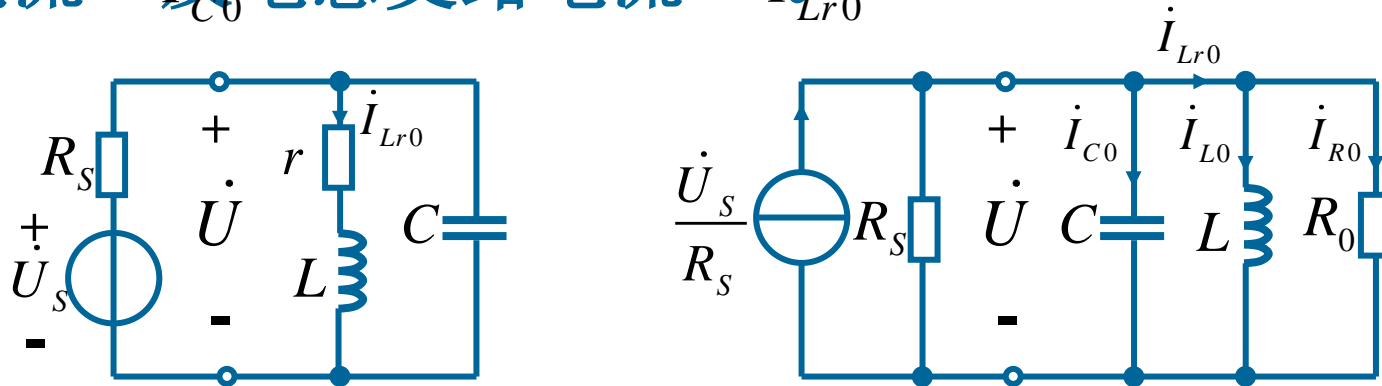


10-11 题图10-11所示并联谐振电路, $L = 0.1mH$, $C = 100pF$, $r = 10\Omega$, $R_s = 100k\Omega$, $\dot{U}_s = 2\angle 0^\circ$, 试求(1)谐振角频率 ω_0 ; (2)端电压 \dot{U} ; (3)整个电路的品质因数 Q' ; (4)谐振时电容支路电流 \dot{I}_{C0} 及电感支路电流 \dot{I}_{Lr0}




解: 这是一个实际的并联谐振电路, 其等效电路如右图所示; 且: $R_0 = \frac{L}{Cr} = 100k\Omega$

$$(1) \quad \omega_0 = \frac{1}{\sqrt{LC}} = 10^7 \text{ rad/s}$$

$$(2) \quad \dot{U} = \frac{U_s}{R_s} \times (R_s // R_0) = 1\angle 0^\circ \text{ V}$$
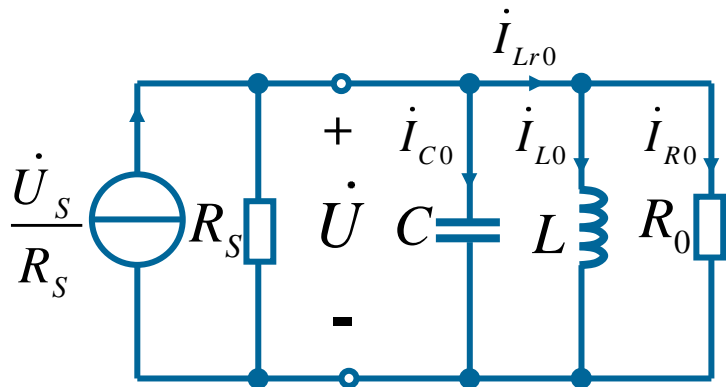
$$(3) \quad Q' = \frac{R_s C}{G} = \omega_0 CR = \omega_0 C(R_s // R_0) = 50$$



$$(4) \quad \dot{I}_{C0} = jQ' \cdot \frac{\dot{U}_s}{R_s} = 1 \angle 90^\circ \text{ mA} \quad (\text{或 } \dot{I}_{C0} = j\omega_0 C \dot{U})$$

$$\dot{I}_{L0} = -\dot{I}_{C0} = 1 \angle -90^\circ \text{ mA}$$

$$\dot{I}_{R0} = \frac{\dot{U}_s}{R_s} \cdot \frac{R_s}{R_s + R_0} = 0.01 \angle 0^\circ \text{ mA}$$

$$\therefore \dot{I}_{Lr0} = \dot{I}_{L0} + \dot{I}_{R0} = 0.01 \angle 0^\circ + 1 \angle -90^\circ = 0.01 - j1 \text{ mA}$$